

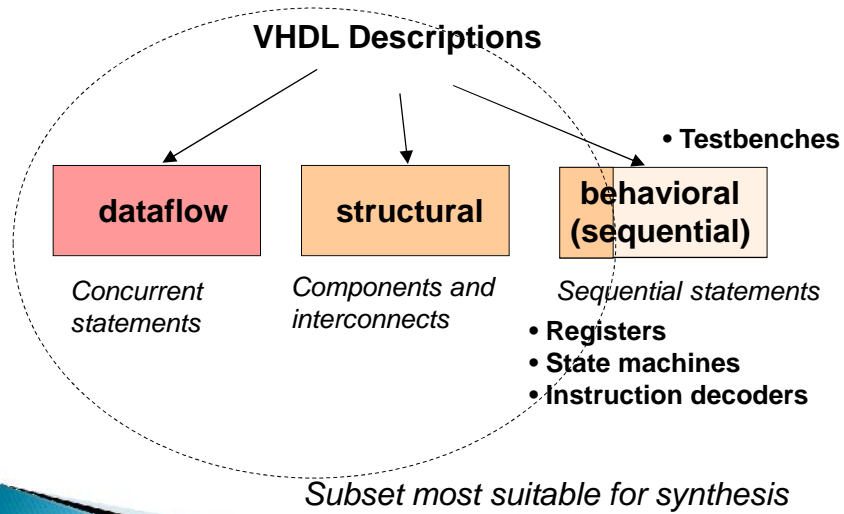


## Types of VHDL Description (Modeling Styles)

### Types of VHDL Description

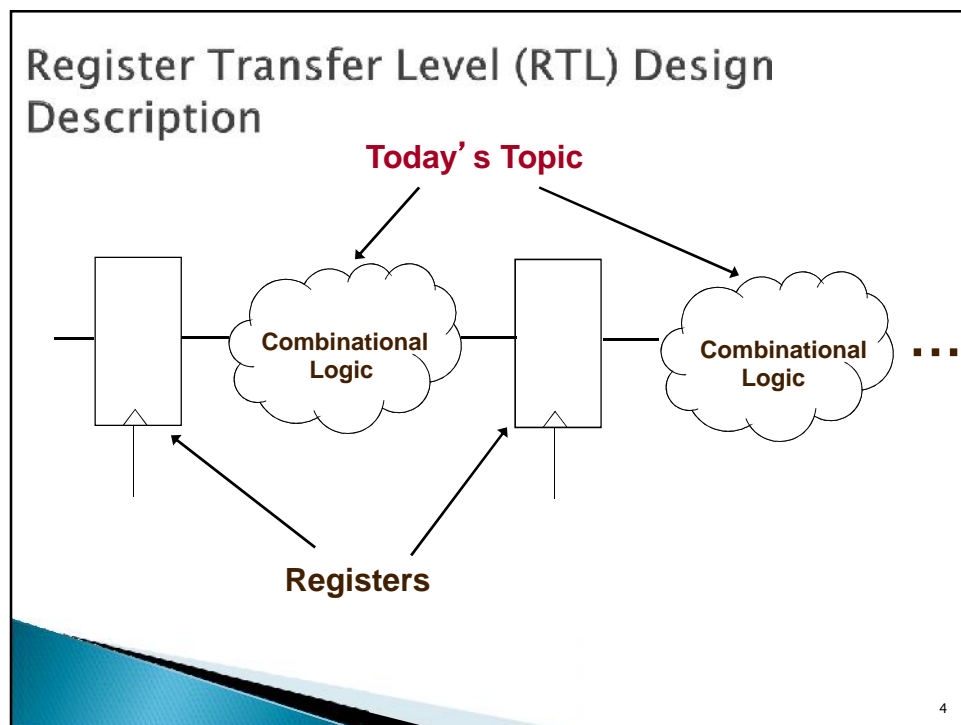

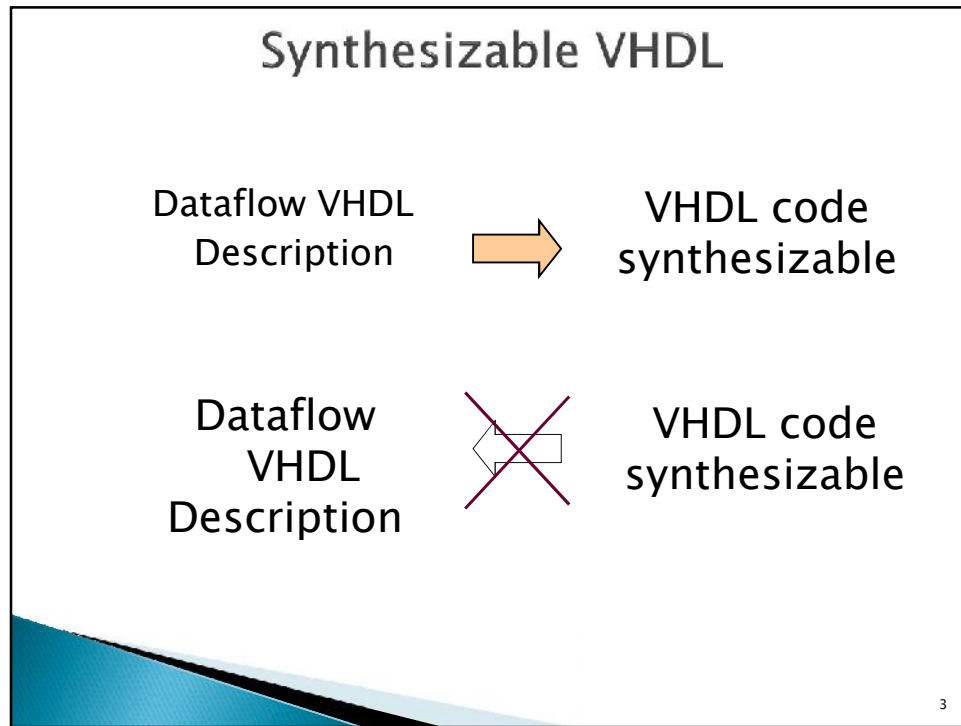

## Data-Flow VHDL

### Concurrent Statements

- simple concurrent signal assignment  
(**Ö**)
- conditional concurrent signal assignment  
(**when-else**)
- selected concurrent signal assignment  
(**with-select-when**)
- generate scheme for equations  
(**for-generate**)

5

## Data-Flow VHDL


### Concurrent Statements

- simple concurrent signal assignment  
(**Ö**)
- conditional concurrent signal assignment  
(**when-else**)
- selected concurrent signal assignment  
(**with-select-when**)
- generate scheme for equations  
(**for-generate**)


6

## Signals

SIGNAL a : STD\_LOGIC;

 


 SIGNAL b : STD\_LOGIC\_VECTOR(7 DOWNTO 0);



7

## Merging wires and buses

 


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);
SIGNAL c: STD_LOGIC;
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);
```

```
d <= a & b & c;
```

8

## Splitting buses

 


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);
SIGNAL c: STD_LOGIC;
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);

a <= d(9 downto 6);
b <= d(5 downto 1);
c <= d(0);
```

9

## Data-flow VHDL: Example

 

## Data-flow VHDL: Example (1)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( x      : IN          STD_LOGIC ;
          y      : IN          STD_LOGIC ;
          cin    : IN          STD_LOGIC ;
          s      : OUT         STD_LOGIC ;
          cout   : OUT         STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE dataflow OF fulladd IS
BEGIN
    s <= x XOR y XOR cin ;
    cout <= (x AND y) OR (cin AND x) OR (cin AND y) ;
END dataflow ;

```

11

## Logic Operators

### ▶ Logic operators

and	or	nand	nor	xor	not	xnor
-----	----	------	-----	-----	-----	------

### ▶ Logic operators precedence

Highest  
↓  
Lowest

and	or	nand	not	nor	xor	xnor
-----	----	------	-----	-----	-----	------

only in VHDL-93  
or later

12

## No Implied Precedence

Wanted:  $y = ab + cd$

### Incorrect


$y \leq a \text{ and } b \text{ or } c \text{ and } d ;$   
 equivalent to  
 $y \leq ((a \text{ and } b) \text{ or } c) \text{ and } d ;$   
 equivalent to  
 $y = (ab + c)d$

### Correct

$y \leq (a \text{ and } b) \text{ or } (c \text{ and } d) ;$

13

 $\text{arith\_result} \leq a + b + c - 1;$



14

## Signal assignment statement with a closed feedback loop

- ▶ A signal appears in both sides of a concurrent assignment statement
- ▶ E.g.,  
**q** <= ((**not q**) and (**not en**)) or (d and en);
- ▶ Syntactically correct
- ▶ Form a closed feedback loop
- ▶ Should be avoided

15

## Data-Flow VHDL

### Concurrent Statements

- simple concurrent signal assignment  
(**Ö**)
- conditional concurrent signal assignment  
(**when-else**)
- selected concurrent signal assignment  
(**with-select-when**)
- generate scheme for equations  
(**for-generate**)


16



## Most often implied structure
 
### When - Else


```
target_signal <= value1 when condition1 else
                value2 when condition2 else
                . . .
                valueN-1 when conditionN-1 else
                valueN;
```



17

 
## 2-to-1 “abstract” mux

- ▶ sel has a data type of boolean
- ▶ If sel is true, the input from “T” port is connected to output.
- ▶ If sel is false, the input from “F” port is connected to output.




18

 
```
signal_name <= value_expr_1 when boolean_expr_1 else
value_expr_2;
```



19

```
signal_name <= value_expr_1 when boolean_expr_1 else
value_expr_2 when boolean_expr_2 else
value_expr_3 when boolean_expr_3 else
value_expr_4;
```

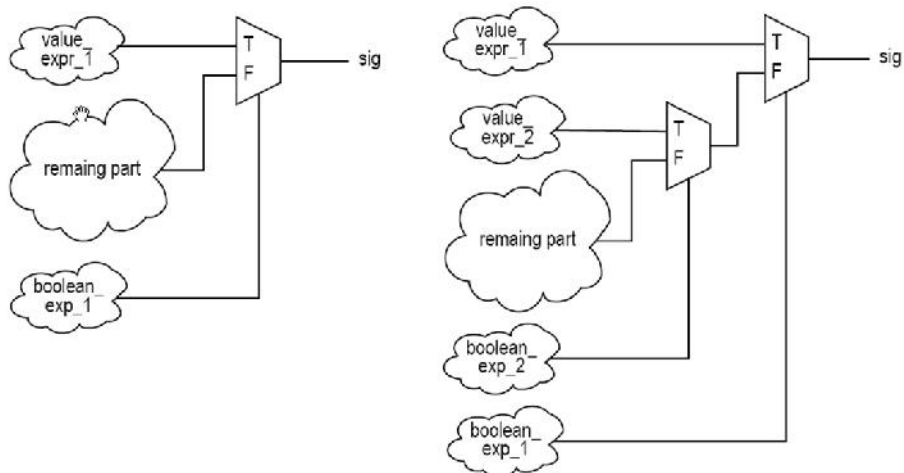2  
0

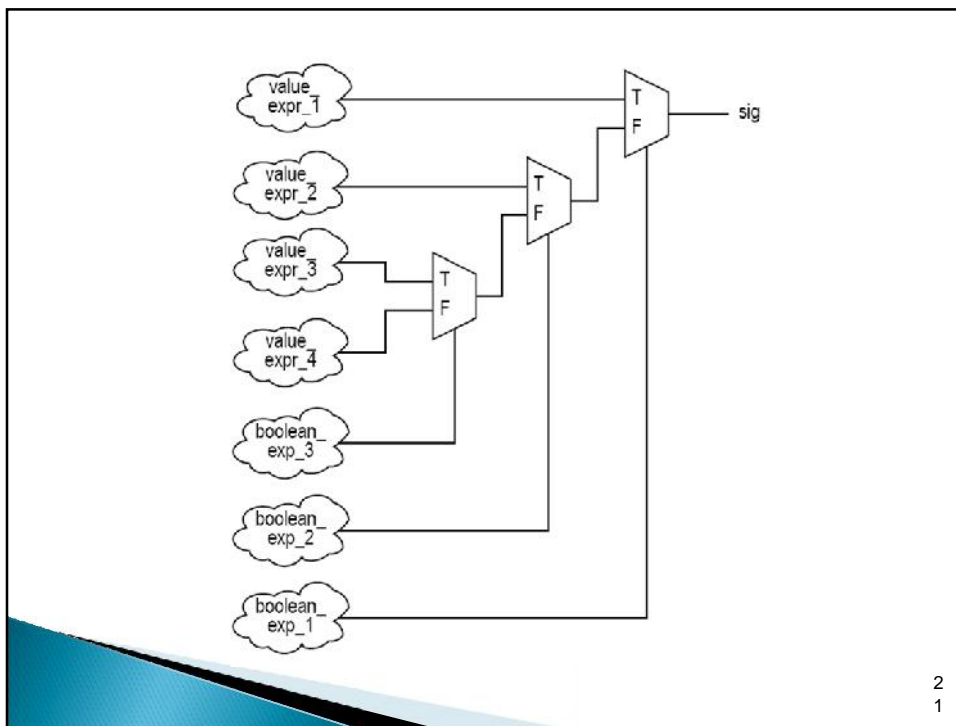


2  
1

• E.g.,


```

signal a,b,c,x,y,r: std_logic;
. . .
r <= a when x=y else
    b when x>y else
    c;

```

 

2  
2

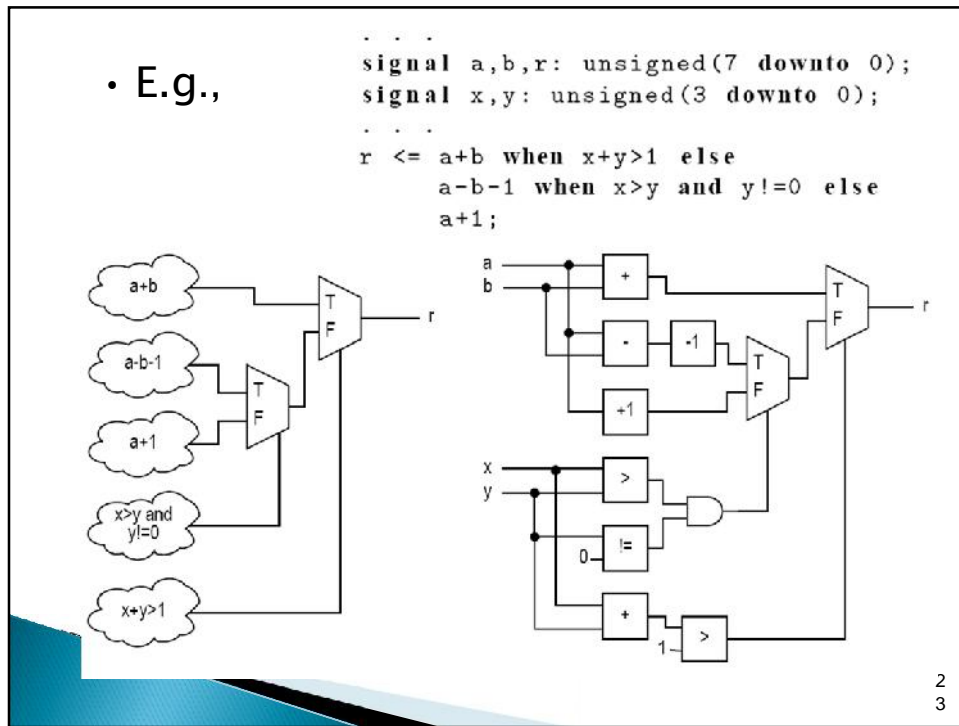

## Signed and Unsigned Types

**Behave** exactly **like**  
**STD\_LOGIC\_VECTOR**

plus, they determine whether a given vector  
should be treated as a signed or unsigned number.

Require

**USE ieee.numeric\_std.all;**

## Operators

- ▶ Relational operators

=	/=	<	<=	>	>=
---	----	---	----	---	----

- ▶ Logic and relational operators precedence

Highest	=	/=	<	<=	>	>=
↓			not			
Lowest	and	or	nand	nor	xor	xnor

25

## Priority of logic and relational operators

compare  $a = bc$

### Incorrect

... when  $a = b$  and  $c$  else ...  
 equivalent to  
 ... when  $(a = b)$  and  $c$  else ...

### Correct

... when  $a = (b \text{ and } c)$  else ...

26

## Data-Flow VHDL

### Concurrent Statements


- **simple concurrent signal assignment**  
(**Ö**)
- **conditional concurrent signal assignment**  
(**when-else**)
- **selected concurrent signal assignment**  
(**with-select-when**)
- **generate scheme for equations**  
(**for-generate**)

27

## Most Often Implied Structure
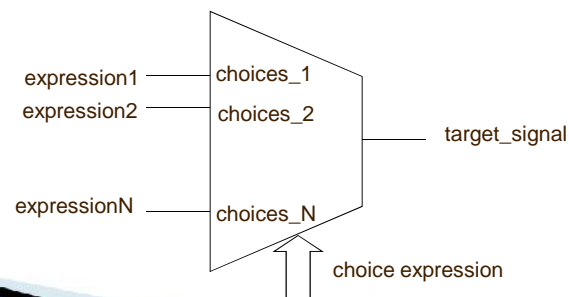
### *With –Select-When*

```
with choice_expression select
  target_signal <= expression1 when choices_1,
                    expression2 when choices_2,
                    . . .
                    expressionN when choices_N;
```



28

## Allowed formats of *choices\_k*

WHEN value

WHEN value\_1 | value\_2 | .... | value N

WHEN OTHERS

```
WITH sel SELECT
    y <= a WHEN "000",
        c WHEN "001" | "111",
        d WHEN OTHERS;
```

29

## Syntax

### ▶ Simplified syntax:

```
with select_expression select
    signal_name <=
        value_expr_1 when choice_1,
        value_expr_2 when choice_2,
        value_expr_3 when choice_3,
        . . .
        value_expr_n when choice_n;
```

30

## Syntax

- ▶ `select_expression`  
Discrete type or 1-D array  
With finite possible values
- ▶ `choice_i`  
A value of the data type
- ▶ Choices must be  
mutually exclusive  
all inclusive  
**others** can be used as last `choice_i`

31

## E.g., 4-to-1 mux

input s	output x
00	a
01	b
10	c
11	d

architecture sel\_arch of mux4 is

begin

    with s select

        x <= a when "00",  
          b when "01",  
          c when "10",  
          d when others;

end sel\_arch ;

    with s select

        x <= a when "00",  
          b when "01",  
          c when "10",  
          d when "11";

32



## E.g., 2-to- $2^2$ binary decoder

```
architecture sel_arch of decoder4 is
begin
  with sel select
    x <= "0001" when "00",
         "0010" when "01",
         "0100" when "10",
         "1000" when others;
end sel_arch ;
```

input s	output x
00	0001
01	0010
10	0100
11	1000

33

## E.g., simple ALU

```
architecture sel_arch of simple_alu is
  signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
  inc <= std_logic_vector(signed(src0)+1);
  sum <= std_logic_vector(signed(src0)+signed(src1));
  diff <= std_logic_vector(signed(src0)-signed(src1));
  with ctrl select
    result <= inc          when "000"|"001"|"010"|"011",
              sum          when "100",
              diff         when "101",
              src0 and src1 when "110",
              src0 or src1  when others;
end sel_arch;
```

input ctrl	output result
0--	src0 + 1
100	src0 + src1
101	src0 - src1
110	src0 and src1
111	src0 or src1

## E.g., Truth table

```

library ieee;
use ieee.std_logic_1164.all;
entity truth_table is
  port(
    a,b: in  std_logic;
    y: out  std_logic
  );
end truth_table;
architecture a of truth_table is
  signal tmp: std_logic_vector(1 downto 0);
begin
  tmp <= a & b;
  with tmp select
    y <= '0' when "00",
        '1' when "01",
        '1' when "10",
        '1' when others; -- "11"
end a;


```

input	output
a b	y
0 0	0
0 1	1
1 0	1
1 1	1

35
 
## Conceptual implementation

- ▶ Achieved by a multiplexing circuit
- ▶ Abstract  $(k+1)$ -to-1 multiplexer
  - sel is with a data type of  $(k+1)$  values:  $c_0, c_1, c_2, \dots, c_k$




```

with select_expression select
  sig <= value_expr_0 when c0,
        value_expr_1 when c1,
        value_expr_n when others;

```

36

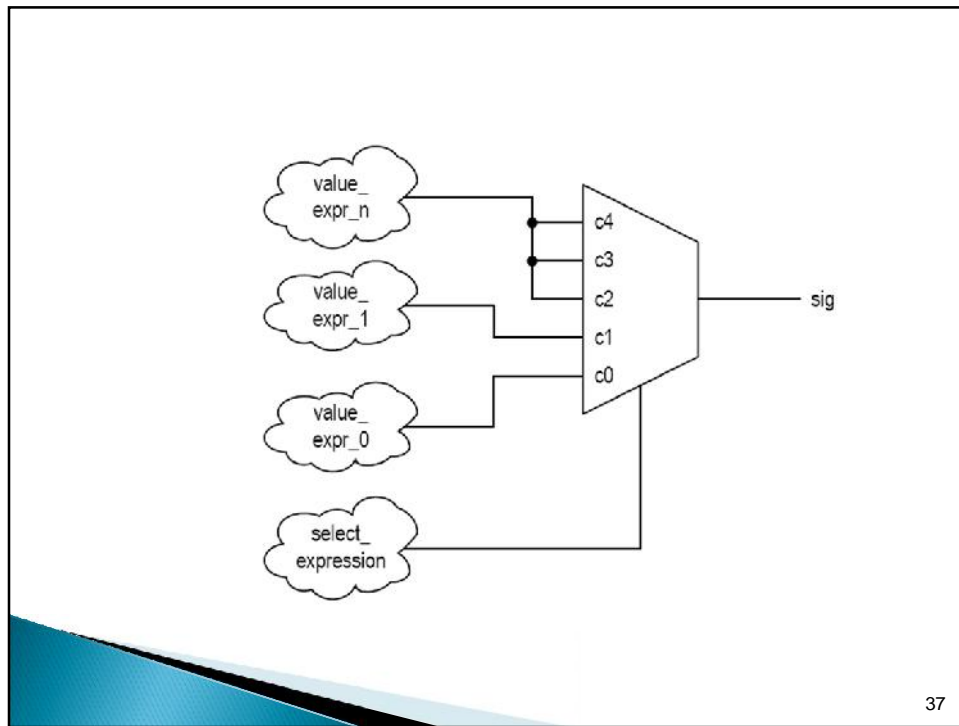


37

▶ E.g.,

```

signal a,b,r: unsigned(7 downto 0);
signal s: std_logic_vector(1 downto 0);
. . .
with s select
    r <= a+1   when "11",
        a-b-1  when "10",
        a+b    when others;

```

 

38

## From selected assignment to conditional assignment

Conversion between conditional vs. selected signal assignment

```

with sel select
    sig <= value_expr_0 when c0,
          value_expr_1 when c1|c3|c5,
          value_expr_2 when c2|c4,
          value_expr_n when others;

sig <=
    value_expr_0 when (sel=c0) else
    value_expr_1 when (sel=c1) or (sel=c3) or (sel=c5) else
    value_expr_2 when (sel=c2) or (sel=c4) else
    value_expr_n;

```

39

## From conditional assignment to selected assignment

```


sig <= value_expr_0 when bool_exp_0 else
      value_expr_1 when bool_exp_1 else
      value_expr_2 when bool_exp_2 else
      value_expr_n;

sel(2) <= '1' when bool_exp_0 else '0';
sel(1) <= '1' when bool_exp_1 else '0';
sel(0) <= '1' when bool_exp_2 else '0';
with sel select
    sig <= value_expr_0 when "100"|"101"|"110"|"111",
          value_expr_1 when "010"|"011",
          value_expr_2 when "001",
          value_expr_n when others;

```

40

## 2-to-1 Multiplexer

 

(a) Graphical symbol

s	f
0	w <sub>0</sub>
1	w <sub>1</sub>

(b) Truth table

41

## VHDL code for a 2-to-1 Multiplexer

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN  STD_LOGIC ;
          f       : OUT STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE dataflow OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END dataflow ;

```

42

## Cascade of two multiplexers

 

43

## VHDL code for a cascade of two multiplexers

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY mux_cascade IS
    PORT ( w1, w2, w3: IN STD_LOGIC ;
          s1, s2      : IN STD_LOGIC ;
          f           : OUT STD_LOGIC ) ;
END mux_cascade ;

ARCHITECTURE dataflow OF mux2to1 IS
BEGIN
    f <= w1 WHEN s1 = '1' ELSE
        w2 WHEN s2 = '1' ELSE
        w3 ;
END dataflow ;

```

44

## 4-to-1 Multiplexer

 

(a) Graphic symbol

$s_1$	$s_0$	$f$
0	0	$w_0$
0	1	$w_1$
1	0	$w_2$
1	1	$w_3$

(b) Truth table

45

## VHDL code for a 4-to-1 Multiplexer

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3 : IN      STD_LOGIC ;
          s                : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          f                : OUT     STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE dataflow OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
            w1 WHEN "01",
            w2 WHEN "10",
            w3 WHEN OTHERS ;
END dataflow ;


```

46

## 2-to-4 Decoder

$En$	$w_1$	$w_0$	$y_3$	$y_2$	$y_1$	$y_0$
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

47

## VHDL code for a 2-to-4 Decoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En : IN      STD_LOGIC ;
          y : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;


ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END dataflow ;

```

48



## Priority Encoder

 

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

49

## VHDL code for a Priority Encoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY priority IS
    PORT ( w : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT   STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT   STD_LOGIC ) ;
END priority ;

ARCHITECTURE dataflow OF priority IS
BEGIN
    y <= "11" WHEN w(3) = '1' ELSE
        "10" WHEN w(2) = '1' ELSE
        "01" WHEN w(1) = '1' ELSE
        "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END dataflow ;

```

50

## Adder mod $2^8$

 

51

## VHDL code for an Adder mod $2^8$

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;


ENTITY adder16 IS
    PORT ( X           : IN    STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Y           : IN    STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          S           : OUT   STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE dataflow OF adder16 IS
BEGIN
    S <= X + Y ;
END dataflow ;

```

52

## 16-bit Unsigned Adder

 

53

## Operations on Unsigned Numbers

For operations on unsigned numbers

USE `ieee.std_logic_unsigned.all`  
and  
signals of the type  
`STD_LOGIC_VECTOR`

OR

USE `ieee.numeric_std.all`,  
signals of the type  
`UNSIGNED`  
and conversion functions:  
`std_logic_vector()`, `unsigned()`

54

## Signed and Unsigned Types

**Behave exactly like  
STD\_LOGIC\_VECTOR**

plus, they determine whether a given vector should be treated as a signed or unsigned number.

Require

**USE ieee.numeric\_std.all;**

55

## VHDL code for a 16-bit Unsigned Adder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN     STD_LOGIC ;
          X             : IN     STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          Y             : IN     STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          S             : OUT    STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          Cout          : OUT    STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE dataflow OF adder16 IS
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNTO 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNTO 0) ;
    Cout <= Sum(16) ;
END dataflow ;
```

56

## Addition of Unsigned Numbers (1)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY adder16 IS
    PORT ( Cin          : IN    STD_LOGIC ;
          X             : IN    STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          Y             : IN    STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          S             : OUT    STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          Cout          : OUT    STD_LOGIC ) ;
END adder16 ;

```

57

## Addition of Unsigned Numbers (2)

```

ARCHITECTURE dataflow OF adder16 IS
    SIGNAL Xu : UNSIGNED(15 DOWNT0 0);
    SIGNAL Yu : UNSIGNED(15 DOWNT0 0);
    SIGNAL Su : UNSIGNED(16 DOWNT0 0) ;
BEGIN
    Xu <= unsigned(X);
    Yu <= unsigned(Y);
    Su <= ('0' & Xu) + Yu + unsigned('0' & Cin) ;
    S <= std_logic_vector(Su(15 DOWNT0 0)) ;
    Cout <= Su(16) ;
END dataflow ;

```

58

## Operations on Signed Numbers

For operations on signed numbers

USE `ieee.std_logic_signed.all`  
and signals of the type  
`STD_LOGIC_VECTOR`

OR

USE `ieee.numeric_std.all`,  
signals of the type  
`SIGNED`,  
and conversion functions:  
`std_logic_vector()`, `signed()`


59

## Unsigned vs. Signed Multiplication

Unsigned			Signed	
1111	15		1111	-1
x 1111	x 15		x 1111	x -1
11100001	225		00000001	1

60

## 8x8-bit Unsigned Multiplier

 

61

## Multiplication of unsigned numbers

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all ;


entity multiply is
  port(
    a : in STD_LOGIC_VECTOR(7 downto 0);
    b : in STD_LOGIC_VECTOR(7 downto 0);
    c : out STD_LOGIC_VECTOR(15 downto 0)
  );
end multiply;

architecture dataflow of multiply is
begin
  c <= a * b;
end dataflow;

```

62

## 8x8-bit Signed Multiplier

 

63

## Multiplication of signed numbers

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_signed.all ;

entity multiply is
  port(
    a : in STD_LOGIC_VECTOR(7 downto 0);
    b : in STD_LOGIC_VECTOR(7 downto 0);
    c : out STD_LOGIC_VECTOR(15 downto 0)
  );
end multiply;


architecture dataflow of multiply is
begin
  c <= a * b;
end dataflow;

```

64


 
## 8x8-bit Unsigned and Signed Multiplier



65

## Multiplication of signed and unsigned numbers

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

entity multiply is
  port(
    a : in STD_LOGIC_VECTOR(7 downto 0);
    b : in STD_LOGIC_VECTOR(7 downto 0);
    cu : out STD_LOGIC_VECTOR(15 downto 0);
    cs : out STD_LOGIC_VECTOR(15 downto 0)
  );
end multiply;


architecture dataflow of multiply is
begin
  -- signed multiplication
  cu <= STD_LOGIC_VECTOR(SIGNED(a)*SIGNED(b));

  -- unsigned multiplication
  cu <= STD_LOGIC_VECTOR(UNSIGNED(a)*UNSIGNED(b));
end dataflow;

```

66

## 4-bit Unsigned Number Comparator

 

67

## VHDL code for a 4-bit **Unsigned** Number Comparator

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY compare IS
    PORT ( A, B          : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          AeqB, AgtB, AltB : OUT  STD_LOGIC ) ;
END compare ;

ARCHITECTURE dataflow OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END dataflow ;

```

68

## VHDL code for a 4-bit Signed Number Comparator

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY compare IS
    PORT ( A, B          : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          AeqB, AgtB, AltB : OUT  STD_LOGIC ) ;
END compare ;

ARCHITECTURE dataflow OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END dataflow ;

```

69

## Arithmetic operations

Synthesizable arithmetic operations:

- ▶ Addition, +
- ▶ Subtraction, -
- ▶ Comparisons, >, >=, <, <=
- ▶ Multiplication, \*
- ▶ Division by a power of 2, /2\*\*6  
(equivalent to right shift)

70

## Arithmetic operations

The result of synthesis of an arithmetic operation is a

- combinational circuit
- without pipelining.

The exact internal **architecture** used (and thus delay and area of the circuit) **may depend** on the **timing constraints** specified during synthesis (e.g., the requested maximum clock frequency).

71

## Integer Types

Operations on signals of the integer types:

**INTEGER, NATURAL,**

and their subtypes, such as

TYPE day\_of\_month IS **RANGE 1 TO 31;**

are synthesizable in the range

$-(2^{31}-1) .. 2^{31} - 1$  for INTEGERS and their subtypes

0 ..  $2^{31} - 1$  for NATURALS and their subtypes

72

## Integer Types

Operations on signals (variables)  
of the integer types:

**INTEGER, NATURAL,**

are less flexible and more difficult to control  
than operations on signals (variables) of the  
type

STD\_LOGIC\_VECTOR


UNSIGNED

SIGNED, and thus

are recommended to be avoided by beginners.

73

## MLU Example MLU Block Diagram

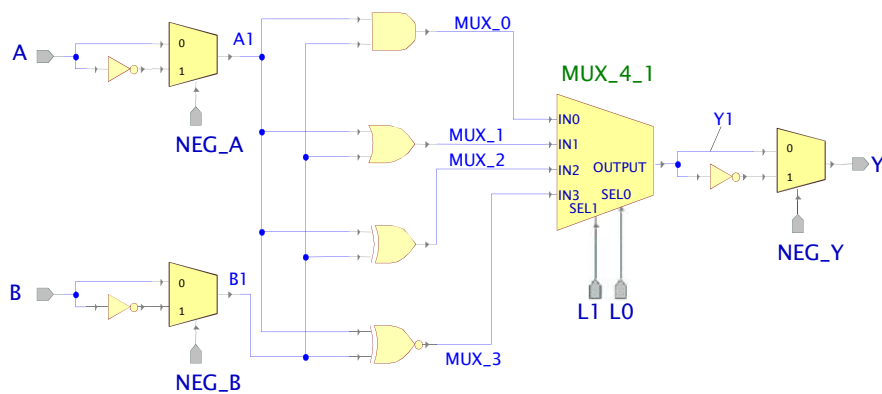

74

## MLU: Entity Declaration

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mlu IS
  PORT(
    NEG_A : IN STD_LOGIC;
    NEG_B : IN STD_LOGIC;
    NEG_Y : IN STD_LOGIC;
    A :    IN STD_LOGIC;
    B :    IN STD_LOGIC;
    L1 :   IN STD_LOGIC;
    L0 :   IN STD_LOGIC;
    Y :    OUT STD_LOGIC
  );
END mlu;
```

75

## MLU: Architecture Declarative Section

```
ARCHITECTURE mlu_dataflow OF mlu IS

  SIGNAL A1 : STD_LOGIC;
  SIGNAL B1 : STD_LOGIC;
  SIGNAL Y1 : STD_LOGIC;
  SIGNAL MUX_0 : STD_LOGIC;
  SIGNAL MUX_1 : STD_LOGIC;
  SIGNAL MUX_2 : STD_LOGIC;
  SIGNAL MUX_3 : STD_LOGIC;
  SIGNAL L : STD_LOGIC_VECTOR(1 DOWNTO 0);
```

76

## MLU – Architecture Body

```
BEGIN
  A1 <= NOT A WHEN (NEG_A='1') ELSE
    A;
  B1 <= NOT B WHEN (NEG_B='1') ELSE
    B;
  Y <= NOT Y1 WHEN (NEG_Y='1') ELSE
    Y1;

  MUX_0 <= A1 AND B1;
  MUX_1 <= A1 OR B1;
  MUX_2 <= A1 XOR B1;
  MUX_3 <= A1 XNOR B1;

  L <= L1 & L0;

  with (L) select
    Y1 <= MUX_0 WHEN "00",
          MUX_1 WHEN "01",
          MUX_2 WHEN "10",
          MUX_3 WHEN OTHERS;

END mlu_dataflow;
```

77

## Combinational Logic Synthesis for Beginners

78

## Simple rules for beginners

For combinational logic,  
use only concurrent statements

- concurrent signal assignment ( $\Leftarrow$ )
- conditional concurrent signal assignment  
(when-else)
- selected concurrent signal assignment  
(with-select-when)
- generate scheme for equations  
(for-generate)

79

## Simple rules for beginners

For circuits composed of

- simple logic operations (logic gates)
- simple arithmetic operations (addition, subtraction, multiplication)
- shifts/rotations by a constant

use

- concurrent signal assignment ( $\Leftarrow$ )

80



## Simple rules for beginners

For circuits composed of

- multiplexers
- decoders, encoders
- tri-state buffers

use

- conditional concurrent signal assignment  
(when-else) (ending with **ELSE**)
- selected concurrent signal assignment  
(with-select-when)  
(ending with **WHEN OTHERS;**)

81

## Example: VHDL code for a 4-to-1 MUX

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3 : IN      STD_LOGIC ;
          s                : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          f                : OUT      STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE dataflow OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
          w1 WHEN "01",
          w2 WHEN "10",
          w3 WHEN OTHERS ;
END dataflow ;

```

82

## when-else vs. with-select-when (1)

"when-else" should be used when:

- 1) there is only one condition (and thus, only one else), as in the 2-to-1 MUX
- 2) conditions are independent of each other (e.g., they test values of different signals)
- 3) conditions reflect priority (as in priority encoder); one with the highest priority need to be tested first.

83

## when-else vs. with-select-when (2)

"with-select-when" should be used when there is

- 1) more than one condition
- 2) conditions are closely related to each other (e.g., represent different ranges of values of the same signal)
- 3) all conditions have the same priority (as in the 4-to-1 MUX).

84

## Left vs. right side of the assignment

**Left side**

<=

**Right side**

<= when-else

with-select <=

- Internal signals (defined in a given architecture)
- Ports of the mode
  - **out**
  - inout

Expressions including:

- Internal signals (defined in a given architecture)
- Ports of the mode
  - **in**
  - inout