

Processes in VHDL

- ▶ Processes Describe Sequential Behavior
- ▶ Processes in VHDL Are Very Powerful Statements
 - Allow to define an arbitrary behavior that may be difficult to represent by a real circuit
 - Not every process can be synthesized
- ▶ Use Processes with Caution in the Code to Be Synthesized
- ▶ Use Processes Freely in Testbenches

3

Anatomy of a Process

OPTIONAL

```
[label:] PROCESS [(sensitivity list)]  
  [declaration part]  
BEGIN  
  statement part  
END PROCESS [label];
```

4

PROCESS with a SENSITIVITY LIST


- ▶ List of signals to which the process is sensitive.
- ▶ Whenever there is an event on any of the signals in the sensitivity list, the process fires.
- ▶ Every time the process fires, it will run in its entirety.
- ▶ **WAIT statements are NOT ALLOWED in a processes with SENSITIVITY LIST.**

```
label: process (sensitivity list)
    declaration part
begin
    statement part
end process;
```

5

Component Equivalent of a Process
 
```
priority: PROCESS (clk)
BEGIN
    IF w(3) = '1' THEN
        y <= "11" ;
    ELSIF w(2) = '1' THEN
        y <= "10" ;
    ELSIF w(1) = c THEN
        y <= a and b;
    ELSE
        z <= "00" ;
    END IF ;
END PROCESS ;
```




- ▶ All signals which appear on the sensitivity list are inputs e.g. *clk*
- ▶ All signals which appear on the left of signal assignment statement (*<=>*) are outputs e.g. *y, z*
- ▶ Note that **not all inputs need to be included on the sensitivity list**
- ▶ All signals which appear on the right of signal assignment statement (*<=>*) or in logic expressions are inputs e.g. *w, a, b, c*

6



D flip-flop


Graphical symbol

 

Truth table

Clk	D	Q(t+1)
↑	0	0
↑	1	1
0	-	Q(t)
1	-	Q(t)

Timing diagram

 

D latch


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q          : OUT  STD_LOGIC ) ;
END latch ;

ARCHITECTURE behavioral OF latch IS
BEGIN
    PROCESS ( D, Clock )
    BEGIN
        IF Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END behavioral ;

```

 

9

D flip-flop


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q          : OUT  STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE behavioral2 OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF rising_edge(Clock) THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END behavioral2 ;

```

 

10


D flip-flop

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q          : OUT  STD_LOGIC );
END flipflop ;

```

 

```

ARCHITECTURE behavioral OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END behavioral ;

```

11


D flip-flop with asynchronous reset

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop_ar IS
    PORT ( D, Resetn, Clock : IN    STD_LOGIC ;
          Q                  : OUT  STD_LOGIC );
END flipflop_ar ;

```

 

```

ARCHITECTURE behavioral OF flipflop_ar IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF rising_edge(Clock) THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END behavioral ;

```

12


D flip-flop with synchronous reset

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY flipflop_sr IS
    PORT ( D, Resetn, Clock : IN      STD_LOGIC ;
          Q : OUT          STD_LOGIC);
END flipflop_sr ;

ARCHITECTURE behavioral OF flipflop_sr IS
BEGIN
    PROCESS(Clock)
    BEGIN
        IF rising_edge(Clock) THEN
            IF Resetn = '0' THEN
                Q <= '0' ;
            ELSE
                Q <= D ;
            END IF ;
        END IF;
    END PROCESS ;
END behavioral ;

```

 

13

Asynchronous vs. Synchronous

- ▶ In the IF loop, asynchronous items are **Before** the rising_edge(Clock) statement
- ▶ In the IF loop, synchronous items are **After** the rising_edge(Clock) statement

14

8-bit register with asynchronous reset


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY reg8 IS
    PORT ( D           : IN    STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, Clock : IN    STD_LOGIC ;
          Q           : OUT   STD_LOGIC_VECTOR(7 DOWNTO 0) );
END reg8 ;

ARCHITECTURE behavioral OF reg8 IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        PROCESS ( Resetn, Clock )
        BEGIN
            IF Resetn = '0' THEN
                Q <= "0000000" ;
            ELSIF rising_edge(Clock) THEN
                Q <= D ;
            END IF ;
        END PROCESS ;
    END PROCESS ;
END behavioral ;

```

 

15

N-bit register with asynchronous reset


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regn IS
    GENERIC ( N : INTEGER := 16 ) ;
    PORT ( D           : IN    STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          Resetn, Clock : IN    STD_LOGIC ;
          Q           : OUT   STD_LOGIC_VECTOR(N-1 DOWNTO 0) );
END regn ;

ARCHITECTURE behavioral OF regn IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        PROCESS ( Resetn, Clock )
        BEGIN
            IF Resetn = '0' THEN
                Q <= (OTHERS => '0') ;
            ELSIF rising_edge(Clock) THEN
                Q <= D ;
            END IF ;
        END PROCESS ;
    END PROCESS ;
END behavioral ;

```

 

16

A word on generics

- ▶ Generics are typically **integer** values
In this class, the entity inputs and outputs should be `std_logic` or `std_logic_vector`
But the generics can be **integer**
- ▶ Generics are given a default value
GENERIC (N : INTEGER := 16) ;
This value can be overwritten when entity is instantiated as a component
- ▶ Generics are very useful when instantiating an often-used component
Need a 32-bit register in one place, and 16-bit register in another
Can use the same generic code, just configure them differently

17

Use of OTHERS

OTHERS stand for any index value that has not been previously mentioned.

`Q <= "00000001"` can be written as `Q <= (0 => '1', OTHERS => '0')`

`Q <= "10000001"` can be written as `Q <= (7 => '1', 0 => '1', OTHERS => '0')`
or `Q <= (7 | 0 => '1', OTHERS => '0')`

`Q <= "00011110"` can be written as `Q <= (4 downto 1 => '1', OTHERS => '0')`

18

Component Instantiation in VHDL-93

```

U1: ENTITY work.regn(behavioral)
      GENERIC MAP (N => 4)
      PORT MAP (D => z ,
                Resetn => reset ,
                Clock => clk,
                Q => t );
  
```

19


N-bit register with enable

```


LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regne IS
  GENERIC ( N : INTEGER := 8 ) ;
  PORT ( D : IN STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
        Enable, Clock : IN STD_LOGIC ;
        Q : OUT STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
END regne ;

 ARCHITECTURE behavioral OF regne IS
BEGIN
  PROCESS (Clock)
  BEGIN
    IF rising_edge(Clock) THEN
      IF Enable = '1' THEN
        Q <= D ;
      END IF ;
    END IF ;
  END PROCESS ;
END behavioral ;
  
```



20

 

21


2-bit up-counter with synchronous reset

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clear, Clock : IN      STD_LOGIC ;
          Q : OUT      STD_LOGIC_VECTOR(1 DOWNTO 0) );
END upcount ;

ARCHITECTURE behavioral OF upcount IS
    SIGNAL Count : std_logic_vector(1 DOWNTO 0);
BEGIN
    upcount: PROCESS ( Clock )
    BEGIN
        IF rising_edge(Clock) THEN
            IF Clear = '1' THEN
                Count <= "00" ;
            ELSE
                Count <= Count + 1 ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count;
END behavioral ;

```

 

22


4-bit up-counter with asynchronous reset (1)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY upcount_ar IS
    PORT ( Clock, Resetn, Enable : IN
          Q : OUT : STD_LOGIC_VECTOR (3) );
END upcount_ar ;

```

 


23

4-bit up-counter with asynchronous reset (2)

```

ARCHITECTURE behavioral OF upcount_ar IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Count <= "0000" ;
        ELSIF rising_edge(Clock) THEN
            IF Enable = '1' THEN
                Count <= Count + 1 ;
            END IF ;
        END IF ;
        Q <= Count ;
    END PROCESS ;
END behavioral ;


```

 


24



Shift register - internal structure

 

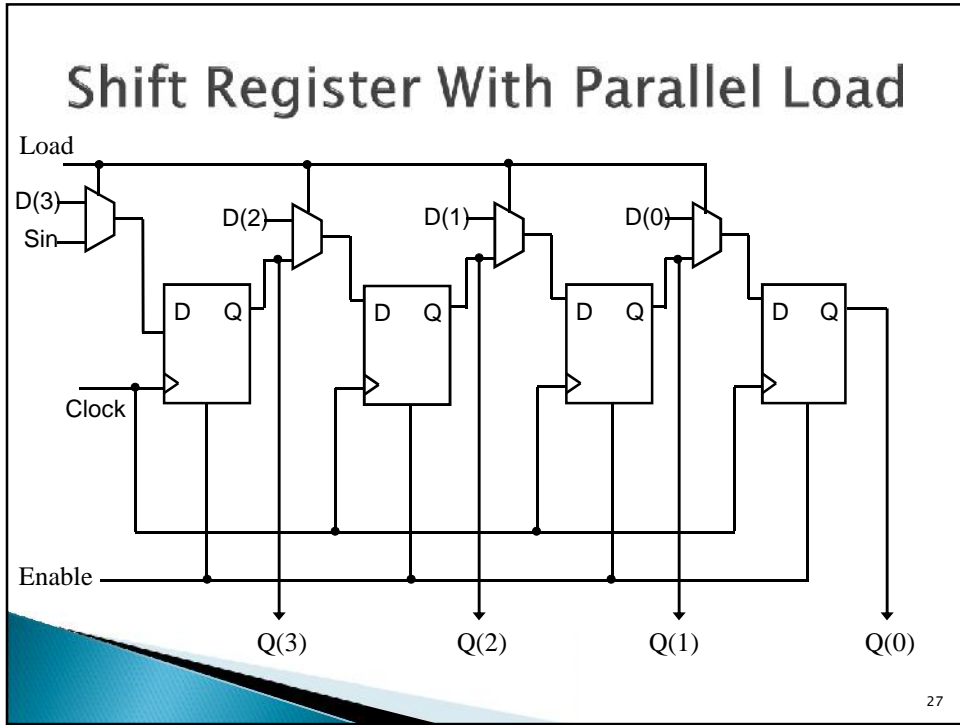


4-bit shift register with parallel load (1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY shift4 IS
```

```
    PORT ( D      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           Enable : IN      STD_LOGIC ;
           Load   : IN      STD_LOGIC ;
           Sin    : IN      STD_LOGIC ;
           Clock  : IN      STD_LOGIC ;
           Q      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
```

```
END shift4 ;
```

 


4-bit shift register with parallel load (2)

```

ARCHITECTURE behavioral OF shift4 IS
    SIGNAL Qt : STD_LOGIC_VECTOR(3 DOWNTO 0);
BEGIN
    PROCESS (Clock)
    BEGIN
        IF rising_edge(Clock) THEN
            IF Enable = '1' THEN
                IF Load = '1' THEN
                    Qt <= D ;
                ELSE
                    Qt <= Sin & Qt(3 downto 1);
                END IF;
            END IF;
        END IF ;
    END PROCESS ;
    Q <= Qt;
END behavioral ;

```

 

29


N-bit shift register with parallel load (1)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY shiftn IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( D : IN STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          Enable : IN STD_LOGIC ;
          Load : IN STD_LOGIC ;
          Sin : IN STD_LOGIC ;
          Clock : IN STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
END shiftn ;

```

 

30


N-bit shift register with parallel load (2)

ARCHITECTURE behavioral OF shiftn IS

```

SIGNAL Qt: STD_LOGIC_VECTOR(N-1 DOWNTO 0);
BEGIN
  PROCESS (Clock)
  BEGIN
    IF rising_edge(Clock) THEN
      IF Enable = '1' THEN
        IF Load = '1' THEN
          Qt <= D ;
        ELSE
          Qt <= Sin & Qt(N-1 downto 1);
        END IF;
      END IF ;
    END PROCESS ;
    Q <= Qt;
  END behavior al;

```

 

31

Sequential Logic Synthesis for Beginners

32

For Beginners

Use processes with very simple structure only to describe


- registers
- shift registers
- counters
- state machines.

Use examples discussed in class as a template.

Create **generic** entities for registers, shift registers, and counters, and instantiate the corresponding components in a higher level circuit using GENERIC MAP PORT MAP.

Supplement sequential components with combinational logic described using concurrent statements.

33

 

34

For Intermediates

1. Use Processes with IF and CASE statements only. Do not use LOOPS or VARIABLES.
2. Sensitivity list of the PROCESS should include **only** signals that can by themselves change the outputs of the sequential circuit (typically, clock and asynchronous set or reset)
3. Do not use PROCESSES without sensitivity list (they can be synthesizable, but make simulation inefficient)

35

For Intermediates (2)

Given a single signal, the assignments to this signal should only be made within a single process block in order to avoid possible conflicts in assigning values to this signal.


Process 1: PROCESS (a, b)

```
BEGIN
  y <= a AND b;
END PROCESS;
```

Process 2: PROCESS (a, b)

```
BEGIN
  y <= a OR b;
END PROCESS;
```

36

 

Constants

Syntax:


CONSTANT name : type := value;

Examples:

```

CONSTANT init_value : STD_LOGIC_VECTOR(3 downto 0) := "0100";
CONSTANT ANDA_EXT : STD_LOGIC_VECTOR(7 downto 0) := X"B4";
CONSTANT counter_width : INTEGER := 16;
CONSTANT buffer_address : INTEGER := 16#FFFE#;
CONSTANT clk_period : TIME := 20 ns;
CONSTANT strobe_period : TIME := 333.333 ms;

```

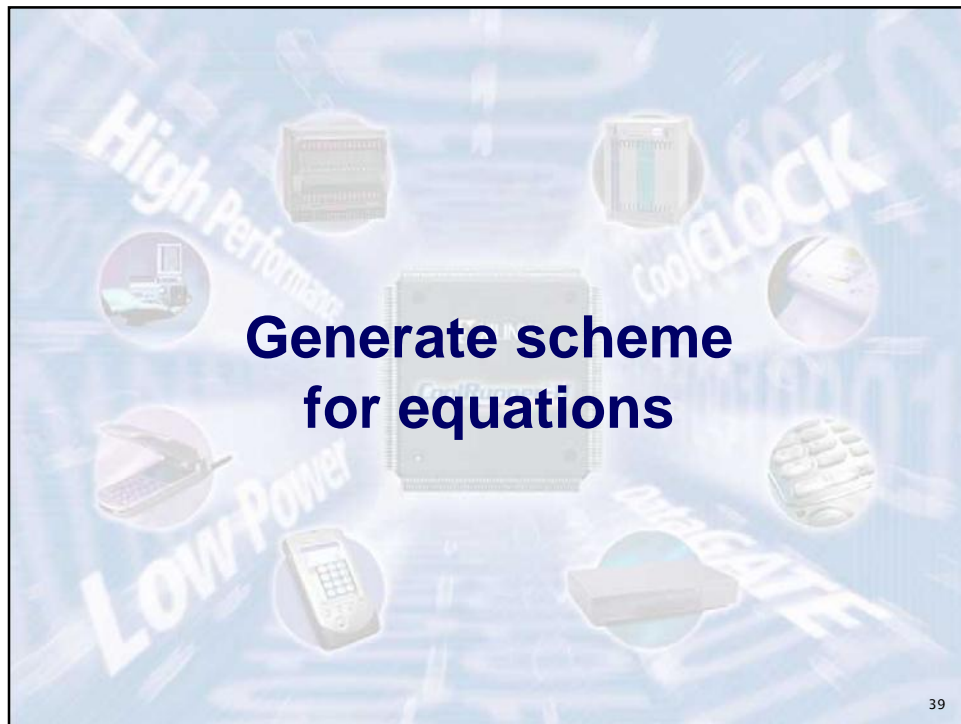

Dataflow VHDL

Major instructions


Concurrent statements

- concurrent signal assignment (\Leftarrow)
- conditional concurrent signal assignment
(when-else)
- selected concurrent signal assignment
(with-select-when)
- **generate scheme for equations**
(**for-generate**)

PARITY Example

41

PARITY: Block Diagram

 


42

PARITY: Entity Declaration

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY parity IS  
  PORT(  
    parity_in  : IN STD_LOGIC_VECTOR(7 DOWNTO 0);  
    parity_out : OUT STD_LOGIC  
  );  
END parity;
```

43

PARITY: Block Diagram

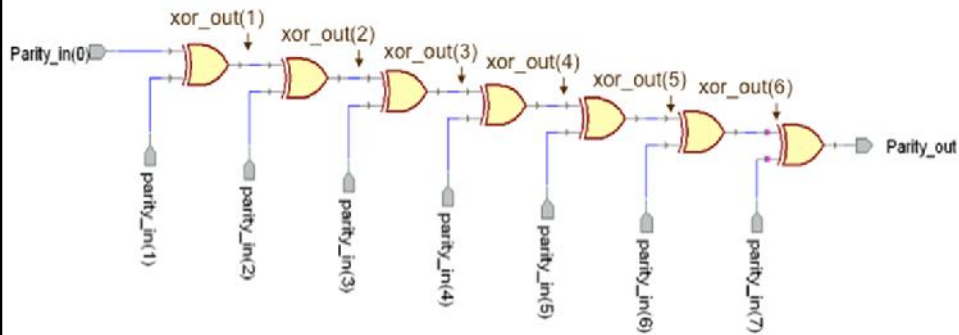

44

PARITY: Architecture

ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: std_logic_vector (6 downto 1);

BEGIN

```
xor_out(1) <= parity_in(0) XOR parity_in(1);
xor_out(2) <= xor_out(1) XOR parity_in(2);
xor_out(3) <= xor_out(2) XOR parity_in(3);
xor_out(4) <= xor_out(3) XOR parity_in(4);
xor_out(5) <= xor_out(4) XOR parity_in(5);
xor_out(6) <= xor_out(5) XOR parity_in(6);
parity_out <= xor_out(6) XOR parity_in(7);
```

END parity_dataflow;

45

PARITY: Architecture (2)

ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: STD_LOGIC_VECTOR (6 DOWNTO 1);


BEGIN

```
G2: FOR i IN 1 TO 7 GENERATE
  left_xor: IF i=1 GENERATE
    xor_out(i) <= parity_in(i-1) XOR parity_in(i);
  END GENERATE;
  middle_xor: IF (i > 1) AND (i < 7) GENERATE
    xor_out(i) <= xor_out(i-1) XOR parity_in(i);
  END GENERATE;
  right_xor: IF i=7 GENERATE
    parity_out <= xor_out(i-1) XOR parity_in(i);
  END GENERATE;
END GENERATE;
```

END parity_dataflow;

46

PARITY: Block Diagram (2)

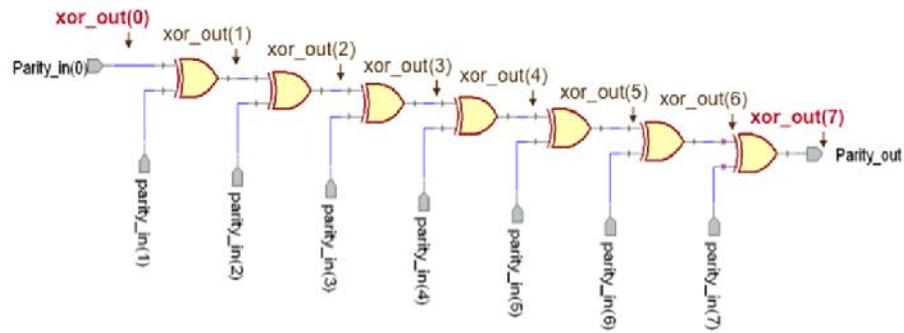

47

PARITY: Architecture

ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: STD_LOGIC_VECTOR (7 downto 0);

BEGIN

```
xor_out(0) <= parity_in(0);
xor_out(1) <= xor_out(0) XOR parity_in(1);
xor_out(2) <= xor_out(1) XOR parity_in(2);
xor_out(3) <= xor_out(2) XOR parity_in(3);
xor_out(4) <= xor_out(3) XOR parity_in(4);
xor_out(5) <= xor_out(4) XOR parity_in(5);
xor_out(6) <= xor_out(5) XOR parity_in(6);
xor_out(7) <= xor_out(6) XOR parity_in(7);
parity_out <= xor_out(7);
```

END parity_dataflow;

48

PARITY: Architecture (2)

```

ARCHITECTURE parity_dataflow OF parity IS
SIGNAL xor_out: STD_LOGIC_VECTOR (7 DOWNTO 0);

BEGIN

    xor_out(0) <= parity_in(0);

    G2: FOR i IN 1 TO 7 GENERATE
        xor_out(i) <= xor_out(i-1) XOR parity_in(i);
    END GENERATE G2;

    parity_out <= xor_out(7);

END parity_dataflow;

```

49

For Generate Statement

For - Generate

```

label:
FOR identifier IN range GENERATE
    {Concurrent Statements}
END GENERATE;

```

if - Generate

```

label:
IF boolean_expression GENERATE
    {Concurrent Statements}
END GENERATE;

```

50



Structural VHDL


Major instructions

- component instantiation (port map)
- component instantiation with generic (generic map, port map)
- **generate scheme for component instantiations (for-generate)**

Example 1

53

Example 1

 

A 4-to-1 Multiplexer

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
  PORT (
    w0, w1, w2, w3 : IN    STD_LOGIC ;
    s               : IN    STD_LOGIC_VECTOR(1 DOWNTO 0) ;
    f               : OUT   STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE Dataflow OF mux4to1 IS
BEGIN
  WITH s SELECT
    f <= w0 WHEN "00",
        w1 WHEN "01",
        w2 WHEN "10",
        w3 WHEN OTHERS ;
END Dataflow ;

```

55

Straightforward code for Example

1

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY Example1 IS
  PORT ( w   : IN    STD_LOGIC_VECTOR(0 TO 15) ;
        s   : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
        f   : OUT   STD_LOGIC ) ;
END Example1 ;

```

56

Straightforward code for Example 1

ARCHITECTURE Structure OF Example1 IS

```

COMPONENT mux4to1
  PORT ( w0, w1, w2, w3 : IN    STD_LOGIC ;
         s              : IN    STD_LOGIC_VECTOR(1 DOWNTO 0) ;
         f              : OUT    STD_LOGIC ) ;
END COMPONENT ;

```

SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;

BEGIN

```

Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNTO 0), m(0) ) ;
Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNTO 0), m(1) ) ;
Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNTO 0), m(2) ) ;
Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNTO 0), m(3) ) ;
Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;
END Structure ;

```

57

Modified code for Example 1

ARCHITECTURE Structure OF Example1 IS

```

COMPONENT mux4to1
  PORT ( w0, w1, w2, w3 : IN    STD_LOGIC ;
         s              : IN    STD_LOGIC_VECTOR(1 DOWNTO 0) ;
         f              : OUT    STD_LOGIC ) ;
END COMPONENT ;

```

SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;

BEGIN

```

G1: FOR i IN 0 TO 3 GENERATE
  Muxes: mux4to1 PORT MAP (
    ..... ) ;
END GENERATE ;
Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;
END Structure ;

```

58

Modified code for Example 1

ARCHITECTURE Structure OF Example1 IS

```

COMPONENT mux4to1
  PORT ( w0, w1, w2, w3 : IN   STD_LOGIC ;
         s               : IN   STD_LOGIC_VECTOR(1 DOWNT0 0) ;
         f               : OUT   STD_LOGIC ) ;
END COMPONENT ;

```

```

SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;

```

BEGIN

```

G1: FOR i IN 0 TO 3 GENERATE
  Muxes: mux4to1 PORT MAP (
    w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 DOWNT0 0), m(i) ) ;
END GENERATE ;

```

```

Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;

```


END Structure ;

59

Example 2

60

Example 2

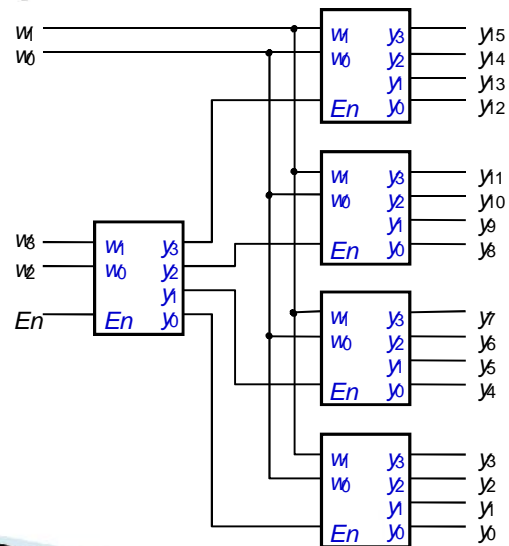

61

A 2-to-4 binary decoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En     : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;

ARCHITECTURE Dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END Dataflow ;

```

62

VHDL code for Example 2 (1)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec4to16 IS
    PORT (w      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          En     : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END dec4to16 ;

```

63

VHDL code for Example 2 (2)

ARCHITECTURE Structure OF dec4to16 IS

```

    COMPONENT dec2to4
        PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
              En     : IN      STD_LOGIC ;
              y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
    END COMPONENT ;

    SIGNAL m : STD_LOGIC_VECTOR(3 DOWNTO 0) ;

BEGIN

    Dec_r0: dec2to4 PORT MAP ( w(1 DOWNTO 0), m(0), y(3 DOWNTO 0) );
    Dec_r1: dec2to4 PORT MAP ( w(1 DOWNTO 0), m(1), y(7 DOWNTO 4) );
    Dec_r2: dec2to4 PORT MAP ( w(1 DOWNTO 0), m(2), y(11 DOWNTO 8) );
    Dec_r3: dec2to4 PORT MAP ( w(1 DOWNTO 0), m(3), y(15 DOWNTO 12) );
    Dec_left: dec2to4 PORT MAP ( w(3 DOWNTO 2), En, m ) ;
END Structure ;

```

64

VHDL code for Example 2 (2)

ARCHITECTURE Structure OF dec4to16 IS

```

COMPONENT dec2to4
  PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        En     : IN      STD_LOGIC ;
        y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END COMPONENT ;

SIGNAL m : STD_LOGIC_VECTOR(3 DOWNTO 0) ;

BEGIN
  G1: FOR i IN 0 TO 3 GENERATE
    Dec_ri: dec2to4 PORT MAP ( ..... , ..... , ..... );
  END GENERATE ;
  Dec_left: dec2to4 PORT MAP ( w(3 DOWNTO 2), En, m ) ;
END Structure ;

```

65

VHDL code for Example 2 (2)

ARCHITECTURE Structure OF dec4to16 IS

```

COMPONENT dec2to4
  PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        En     : IN      STD_LOGIC ;
        y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END COMPONENT ;

SIGNAL m : STD_LOGIC_VECTOR(3 DOWNTO 0) ;

BEGIN
  G1: FOR i IN 0 TO 3 GENERATE
    Dec_ri: dec2to4 PORT MAP ( w(1 DOWNTO 0), m(i), y(4*i+3 DOWNTO 4*i) );
  END GENERATE ;
  Dec_left: dec2to4 PORT MAP ( w(3 DOWNTO 2), En, m ) ;
END Structure ;

```


66

Example 3

Up-or-down Free Running Counter

67

Up-or-down Free Running Counter

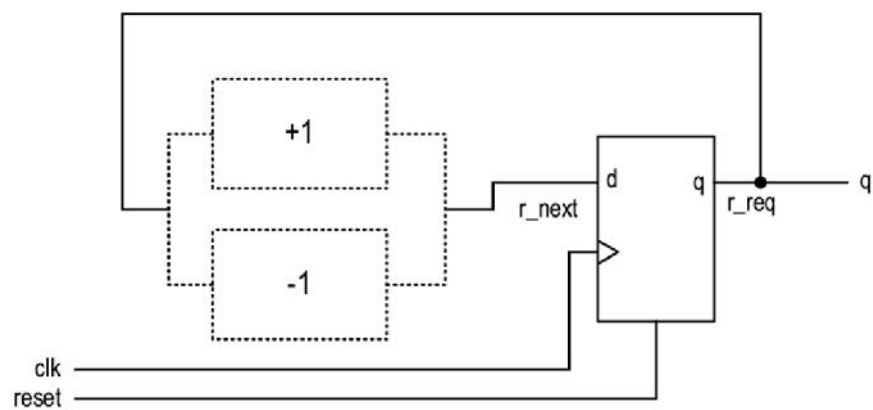

68

Up-or-down Free Running Counter (1)

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity up_or_down_counter is
  generic(
    WIDTH: natural:=4;
    UP: natural:=0
  );
  port(
    clk, reset: in std_logic;
    q: out std_logic_vector(WIDTH-1 downto 0)
  );
end up_or_down_counter;

```

69

Up-or-down Free Running Counter (2)

```

architecture mixed of up_or_down_counter is

  signal r_reg: unsigned(WIDTH-1 downto 0);
  signal r_next: unsigned(WIDTH-1 downto 0);

begin
  -- register
  process(clk,reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;

```

70

Up-or-down Free Running Counter (3)

```
-- next-state logic
inc_gen: -- incrementor
if UP=1 generate
    r_next <= r_reg + 1;
end generate;

dec_gen: --decrementor
if UP/=1 generate
    r_next <= r_reg - 1;
end generate;

-- output logic
q <= std_logic_vector(r_reg);


end mixed;
```

71

Example 4 Up-**and**-down Free Running Counter

72

Up-and-down Free Running Counter

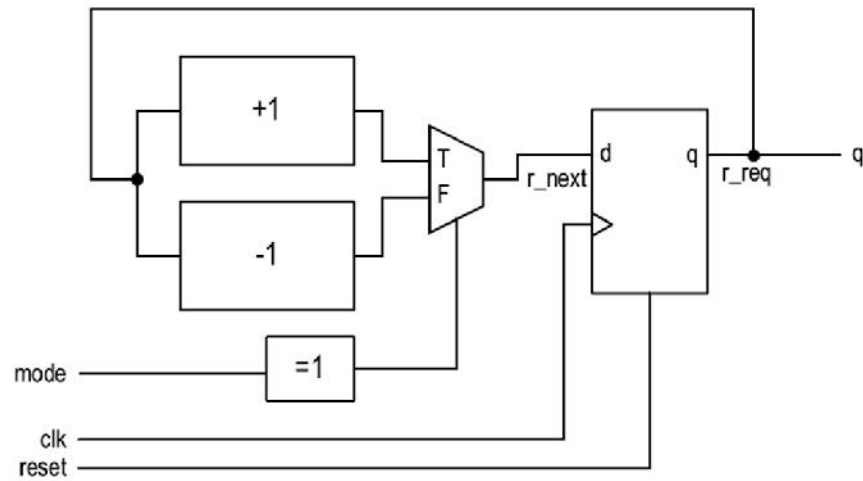

73

Up-and-down Free Running Counter (1)

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity up_and_down_counter is
  generic(WIDTH: natural:=4);
  port(
    clk, reset: in std_logic;
    mode: in std_logic;
    q: out std_logic_vector(WIDTH-1 downto 0)
  );
end up_and_down_counter;

```

74

Up-and-down Free Running Counter (2)

architecture arch of up_and_down_counter is

```
signal r_reg: unsigned(WIDTH-1 downto 0);
signal r_next: unsigned(WIDTH-1 downto 0);
```

```
begin
  -- register
  process(clk,reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
```

75

Up-and-down Free Running Counter (3)

```
-- next-state logic
```

```
r_next <= r_reg + 1 when mode='1' else  
      r_reg - 1;
```

```
-- output logic
```

```
q <= std_logic_vector(r_reg);
```

```
end arch;
```

76